Interfacing Servo Motor with AVR (Firebird V)

Joel M. Pinto and Vishal H. Rajai eYantra Summer Internship'14 Embedded Real-Time Systems Lab Indian Institute of Technology, Bombay

> IIT Bombay July 21, 2014





Agenda of Discussion

- Introduction
- Servo motor
 - Principle and Working
 - Operating Servo Motor
 - Selection of Servo motor
- 3 AVR ATmega2560
 - Generating PWM signals
 - Code





Prerequisite knowledge

- Basic IO Interfacing using ports
- Working with Timers and basic knowledge of registers of ATmega2560.





Introduction

- Servo motors (or servos) are self-contained devices that rotate or push parts of a machine with great precision.
- Servos can put out about 42 oz/in of torque.
- Relatively inexpensive.
- Widely used for educational purpose in mechatronics as they can be controlled by a microcontroller.





A servo mainly contains:





- A servo mainly contains:
 - dc motor





- A servo mainly contains:
 - dc motor
 - gear train





- A servo mainly contains:
 - dc motor
 - gear train
 - potentiometer





- A servo mainly contains:
 - dc motor
 - gear train
 - potentiometer
 - control circuitry.






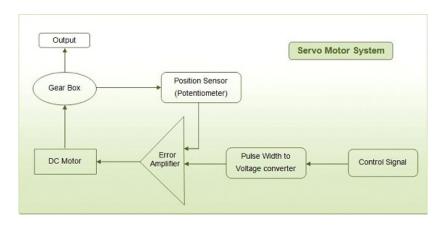- A servo mainly contains:
 - dc motor
 - gear train
 - potentiometer
 - control circuitry.
- Forming closed loop control system.











Principle and Working Operating Servo Motor Selection of Servo motor

 As shown in figure, control signal and output signal are fed to error detector.





Principle and Working Operating Servo Motor

- As shown in figure, control signal and output signal are fed to error detector.
- Resultant signal from error detector acts as input to the dc motor to rotate.





Principle and Working Operating Servo Motor Selection of Servo moto

- As shown in figure, control signal and output signal are fed to error detector.
- Resultant signal from error detector acts as input to the dc motor to rotate.
- Also rotating the potentiometer knob coupled with its shaft via gears.





- As shown in figure, control signal and output signal are fed to error detector.
- Resultant signal from error detector acts as input to the dc motor to rotate.
- Also rotating the potentiometer knob coupled with its shaft via gears.
- Reaching desired angle, there would not be any difference in the signals fed to error detector.






- As shown in figure, control signal and output signal are fed to error detector.
- Resultant signal from error detector acts as input to the dc motor to rotate.
- Also rotating the potentiometer knob coupled with its shaft via gears.
- Reaching desired angle, there would not be any difference in the signals fed to error detector.
- Resulting in motor to stop rotating and wait at that position





Operating servo motor

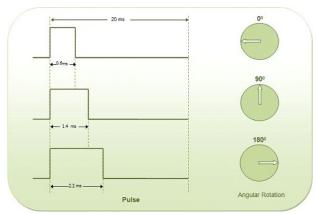• 'on-time' of a PWM signal is used as control signal to rotate motor at particular angle.







 This time period depends on the servo used and not on total time period or duty cycle of PWM signal.





- This time period depends on the servo used and not on total time period or duty cycle of PWM signal.
- Values of on-time for rotating servo to 0 and 180 degree are provided by the manufacturer in data sheet.





- This time period depends on the servo used and not on total time period or duty cycle of PWM signal.
- Values of on-time for rotating servo to 0 and 180 degree are provided by the manufacturer in data sheet.
- Graph of on-time period vs. angle is linear.





- This time period depends on the servo used and not on total time period or duty cycle of PWM signal.
- Values of on-time for rotating servo to 0 and 180 degree are provided by the manufacturer in data sheet.
- Graph of on-time period vs. angle is linear.
- Range of PWM frequency for operating servo is 40-60 Hz









Servo is selected based on its:

Torque





- Torque
- Speed





- Torque
- Speed
- Weight






- Torque
- Speed
- Weight
- Dimensions





Servo connector

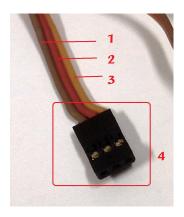


- 1- Ground
- 2- Power
- 3- Control signal
- 4- Connector to controller






Interfacing servo with Firebird V

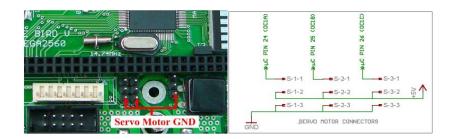





Using Timer1 for PWM generation

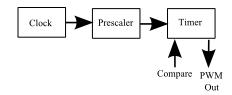

- Timer1 in Fast PWM mode is used here.
- Fast PWM in mode 14 is used to rotate servo motor.

11	1	0	1	1	PWM, Phase Correct	OCRnA	TOP	воттом
12	1	1	0	0	CTC	ICRn	Immediate	MAX
13	1	1	0	1	(Reserved)	-	-	-
14	1	1	1	0	Fast PWM	ICRn	воттом	TOP
15	1	1	1	1	Fast PWM	OCRnA	воттом	TOP

WGM bit description





Counter counts from BOTTOM=0 to TOP





- Counter counts from BOTTOM=0 to TOP
- And sets the output as high till compare value is greater than counter value





- Counter counts from BOTTOM=0 to TOP
- And sets the output as high till compare value is greater than counter value
- Clears the output when the count value matches the value in compare register till the next cycle starts.





- Counter counts from BOTTOM=0 to TOP
- And sets the output as high till compare value is greater than counter value
- Clears the output when the count value matches the value in compare register till the next cycle starts.
- Let the Prescaler, N=256





- Counter counts from BOTTOM=0 to TOP
- And sets the output as high till compare value is greater than counter value
- Clears the output when the count value matches the value in compare register till the next cycle starts.
- Let the Prescaler, N=256
- $f_{cpu} = 14745600 Hz$





• TOP is calculated from desired PWM frequency as:





• TOP is calculated from desired PWM frequency as:

$$f_{PWM} = \frac{f_{cpu}}{N*(1+TOP)}$$

So, $TOP = \frac{f_{cpu}}{N*f_{PWM}} - 1 = 1023$





TOP is calculated from desired PWM frequency as:

$$f_{PWM} = rac{f_{cpu}}{N*(1+TOP)}$$

So, $TOP = rac{f_{cpu}}{N*f_{PWM}} - 1 = 1023$

- ICR1=TOP
- Value of channel A of OCR register will be:





TOP is calculated from desired PWM frequency as:

$$f_{PWM} = \frac{f_{cpu}}{N*(1+TOP)}$$

So, $TOP = \frac{f_{cpu}}{N*f_{PWM}} - 1 = 1023$

- ICR1=TOP
- Value of channel A of OCR register will be:

$$OCR1A = T_{on}(\frac{f_{cpu}}{N}) = T_{on} * 57600$$





TOP is calculated from desired PWM frequency as:

$$f_{PWM} = rac{f_{cpu}}{N*(1+TOP)}$$

So, $TOP = rac{f_{cpu}}{N*f_{PWM}} - 1 = 1023$

- ICR1=TOP
- Value of channel A of OCR register will be: $OCR1A = T_{on}(\frac{f_{cpu}}{N}) = T_{on} * 57600$
- Values of registers like TCCR1A/B and TCNT1 can be found using ATmega2560 datasheet.





```
Header files
```



Header files

```
#define F_CPU 14745600
#include <avr/io.h>
#include <avr/interrupt.h>
#include <util/delay.h>
```





Header files

#define F_CPU 14745600
#include <avr/io.h>
#include <avr/interrupt.h>
#include <util/delay.h>

Port Initialization



Header files

```
#define F_CPU 14745600
#include <avr/io.h>
#include <avr/interrupt.h>
#include <util/delay.h>
```

Port Initialization

```
void port_init()
{
DDRB = DDRB | 0x20;
PORTB = PORTB | 0x20;
}
```

Convert the degrees in terms of counts for Timer1 As the relation between on-time period and corresponding degree is linear, so is the relation between the count value in OCR and degree.





Convert the degrees in terms of counts for Timer1 As the relation between on-time period and corresponding degree is linear, so is the relation between the count value in OCR and degree.

```
float regval = ((float)degrees * 0.512) + 34.56;
OCR1A = (uint16_t) regval;
```





Thank You!

Post your queries on: helpdesk@e-yantra.org



